

# Three-Level Neutral-Point-Clamped Quasi-Z-Source Inverter as a New Solution for Renewable Energy Application

Oleksandr Husev

# Partners



**Tallinn University of Technology**  
Tallinn, Estonia  
D. Vinnikov, O. Husev




**University of Extremadura, Spain**  
E. Romero-Cadaval,  
C. Roncero-Clemente.




**Chernihiv State Technological University, Ukraine**  
S. Stepenko
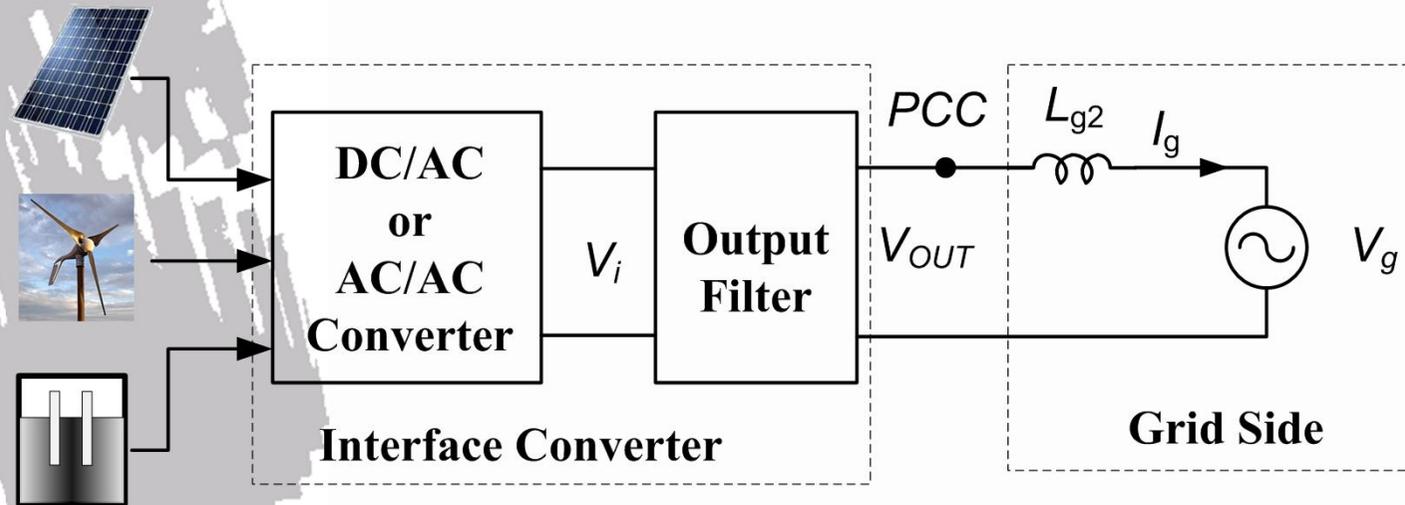
# Introduction: renewable energy applications




# Introduction: traditional solutions

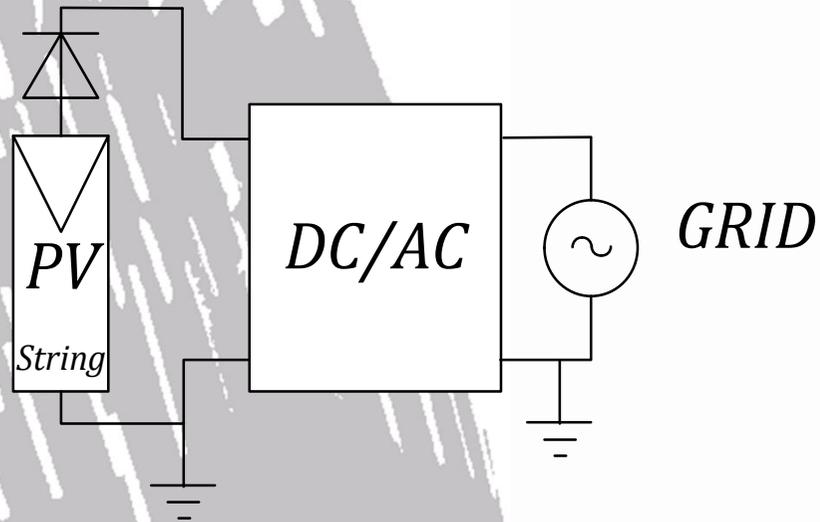


- Simple and cheap solutions
- **Narrow range input voltage operation**


## Maximum Modulation Index

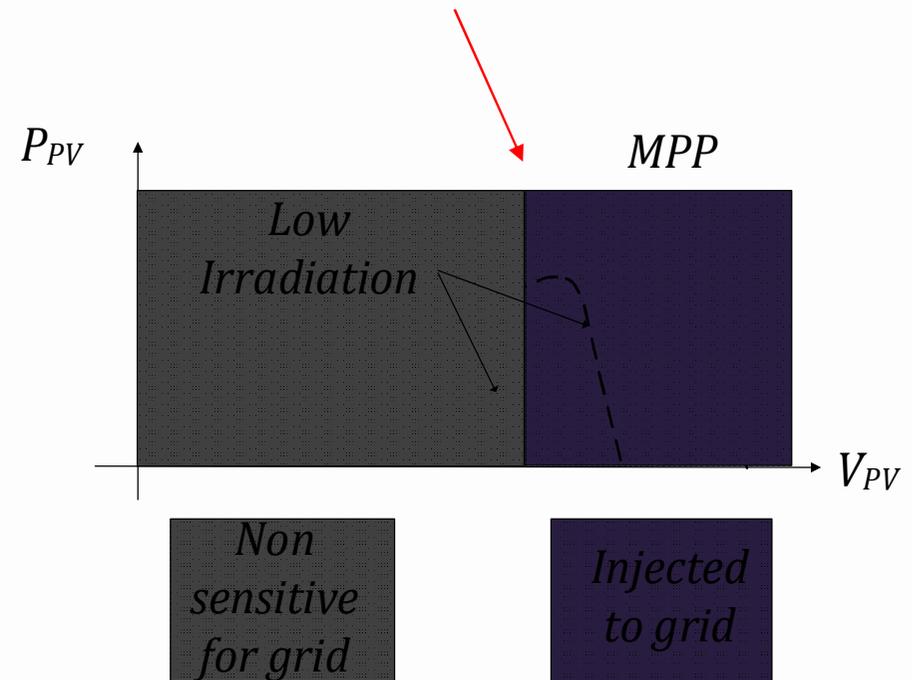

# Introduction: traditional solutions

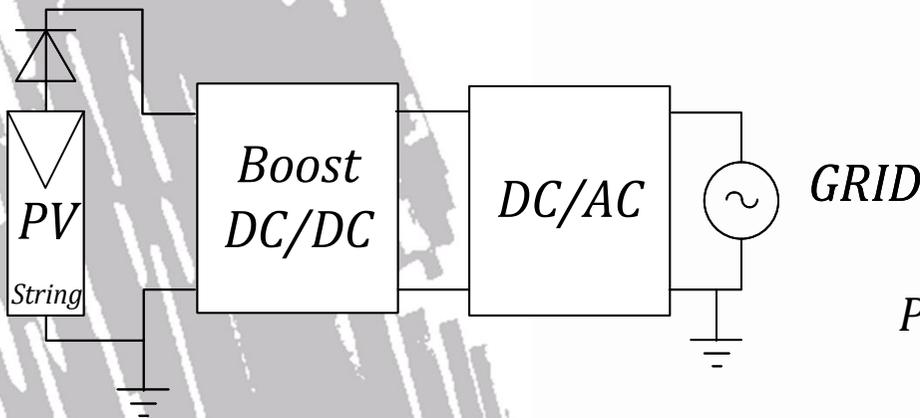

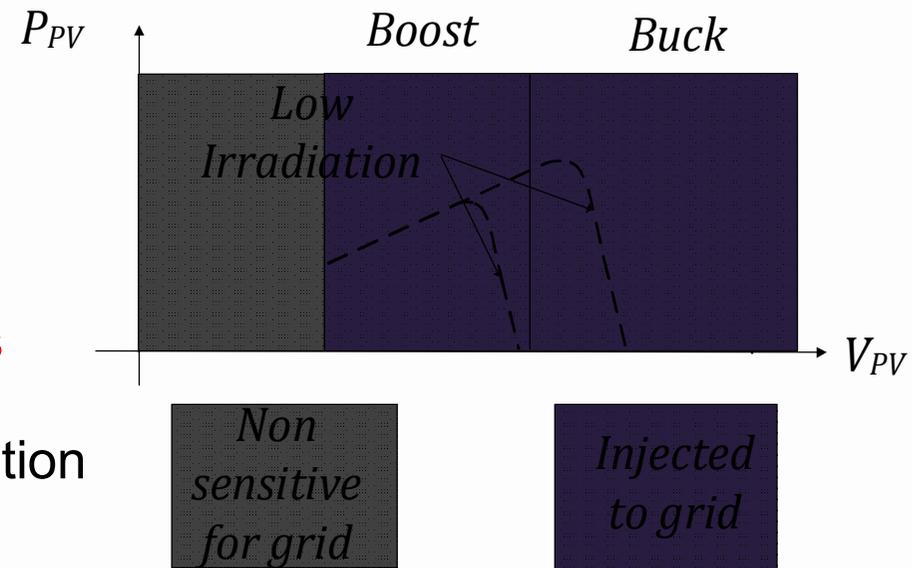
- Two stage conversion solutions
- Wide range input voltage operation



# Introduction: new trends in PV inverters

- Wide range input operation;
- Input current continuous operation mode;
- Bidirectional operations (for heating);
- Active filtering function in PCC;
- Multilevel inverters;
- Integrated boost and buck solutions.


# Introduction: new solutions

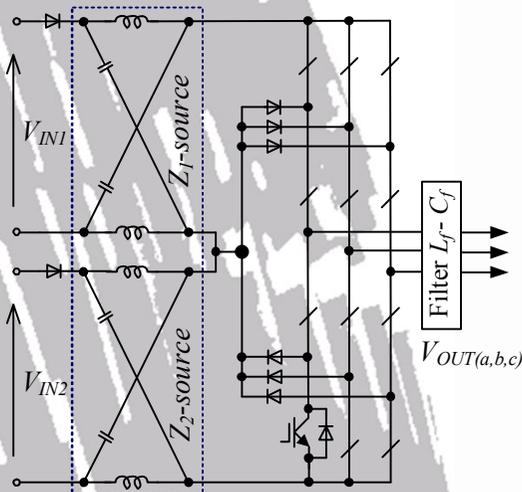


Single-stage buck-boost  
multilevel inverter with  
two separate Z-source  
networks

Poh Chiang Loh; Feng Gao; Blaabjerg, F.; Shi Yun Charmaine Feng; Kong Ngai Jamies Soon, "Pulsewidth-Modulated Z-Source Neutral-Point-Clamped Inverter"

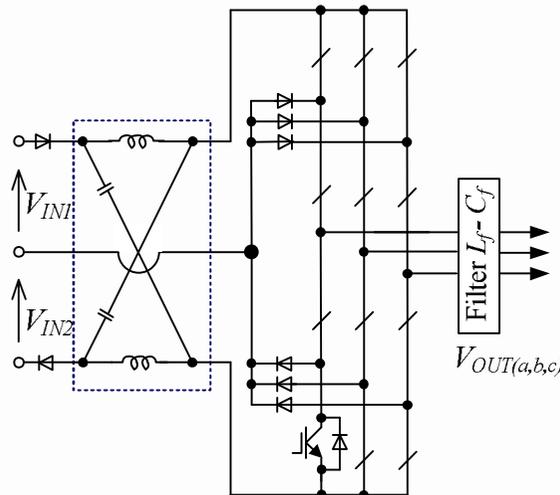Z-source NPC inverter  
with single  
impedance network



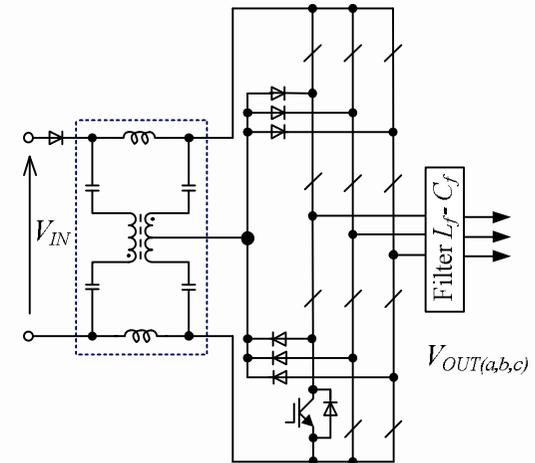Poh Chiang Lo, Sok Wei Lim, Feng Gao, Frede Blaabjerg, "Three-Level Z-Source Inverters Using a Single LC Impedance Network"




NPC inverter with  
single impedance  
network

Strzelecki, R., "Three-Level Z-Source Neutral-Point-Clamped Inverter,"


# Proposed Topology

## 3L-NPC

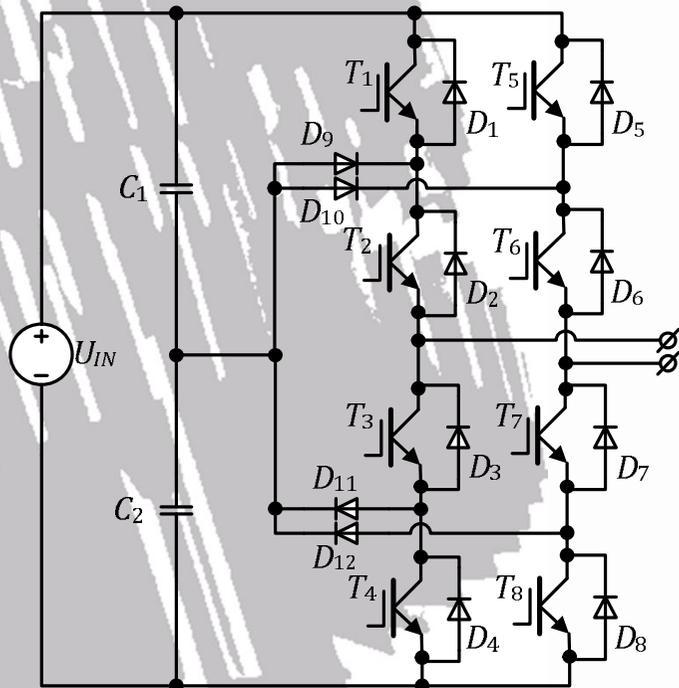


Three-Level Neutral Point Clamped

## 2L-qZS

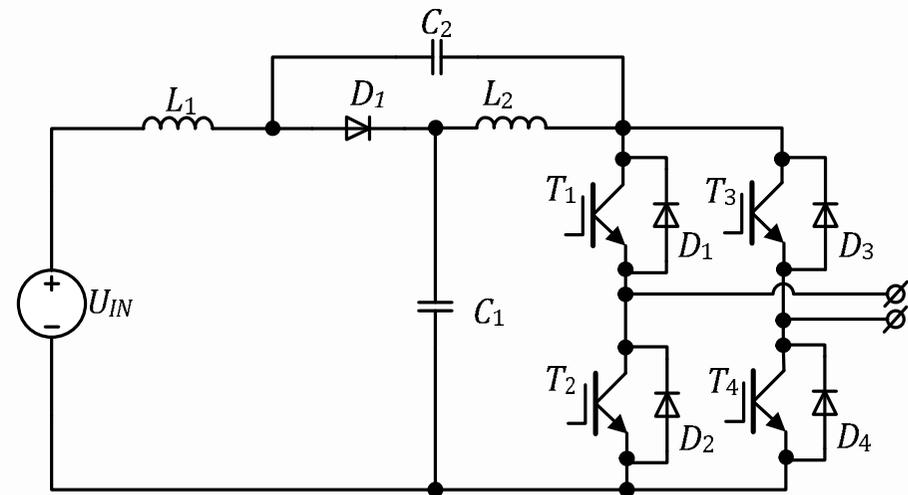

Two-Level Quasi-Z-Source Inverter

# Proposed Topology 3L-NPC-qZSI

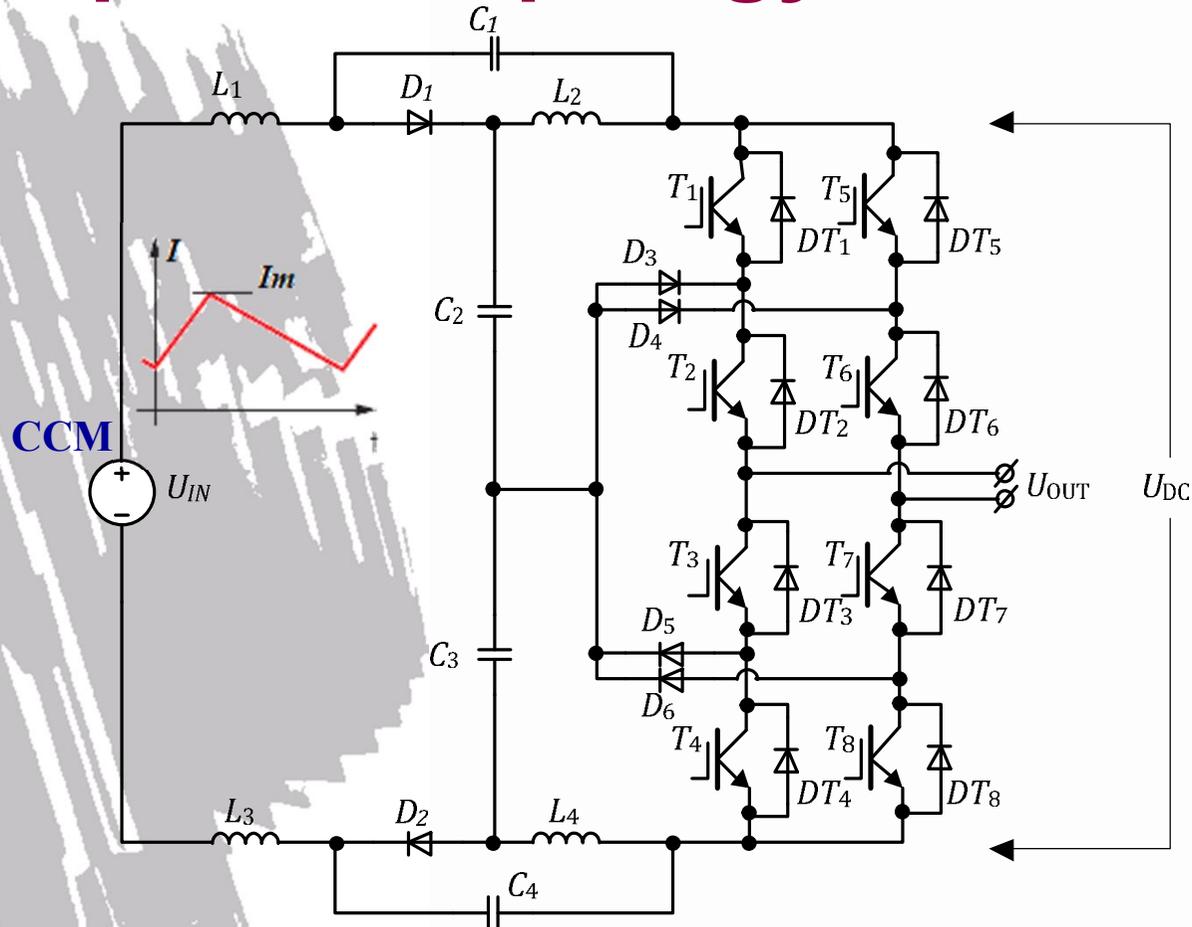


Three-Level Neutral Point Clamped Quasi-Z-Source Inverter

# Proposed Topology: expected benefits

- One stage energy conversion topology;
- Short circuit immunity;
- Low voltage stress on the semiconductors;
- Bidirectional operations (for heating);
- Improved injected current quality;
- Active filtering functions in PCC.

# Proposed Topology 3L-NPC-qZSI

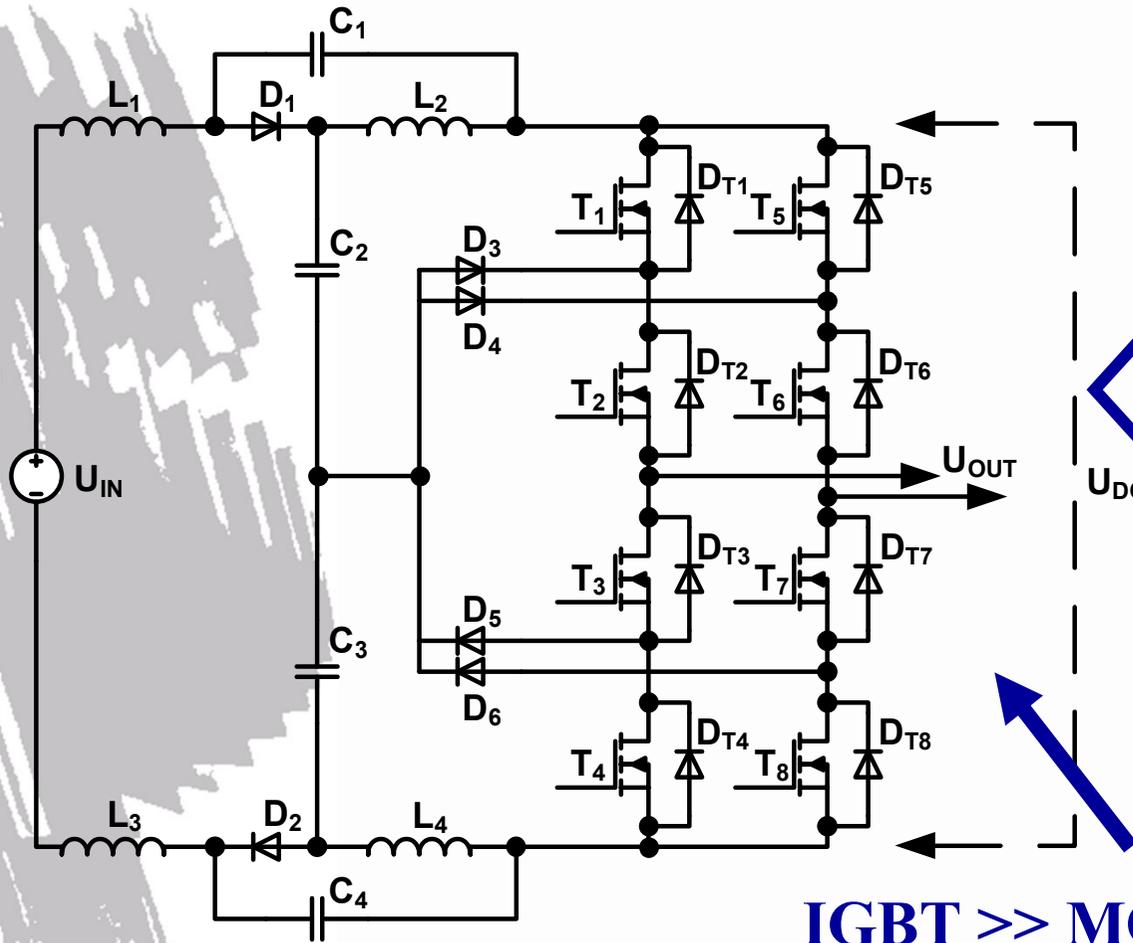


?

Modulation Technique


IGBT >> MOSFET

# Modulation Technique

## 3L-NPC-qZSI

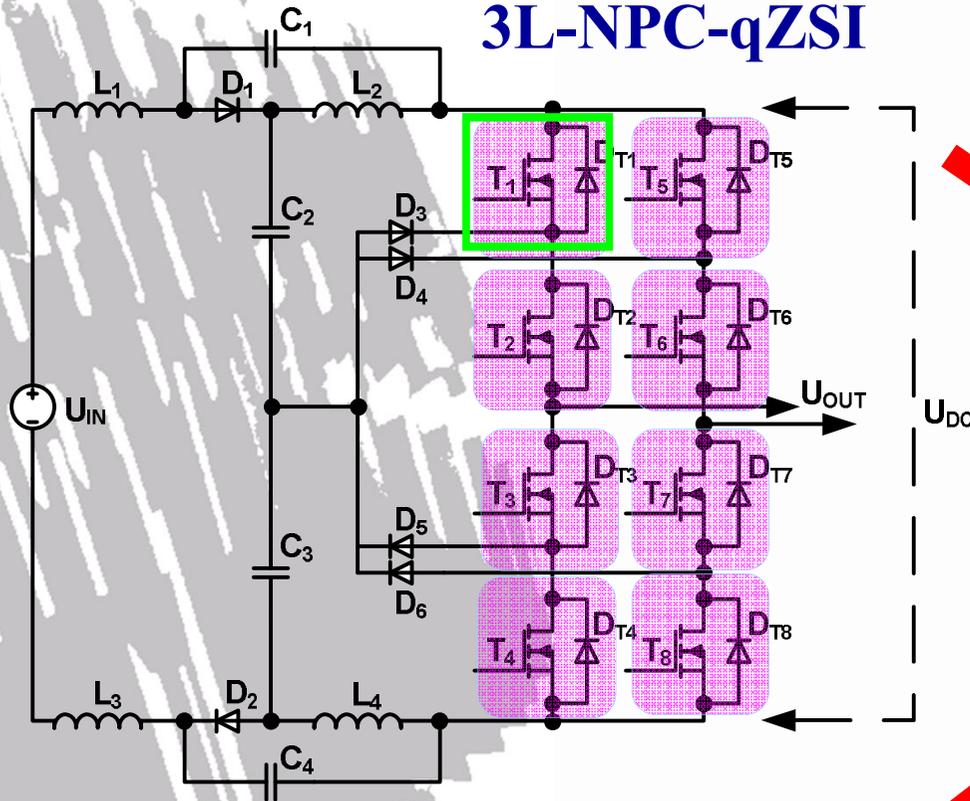

Shoot-through Mode ( $t_s$ )



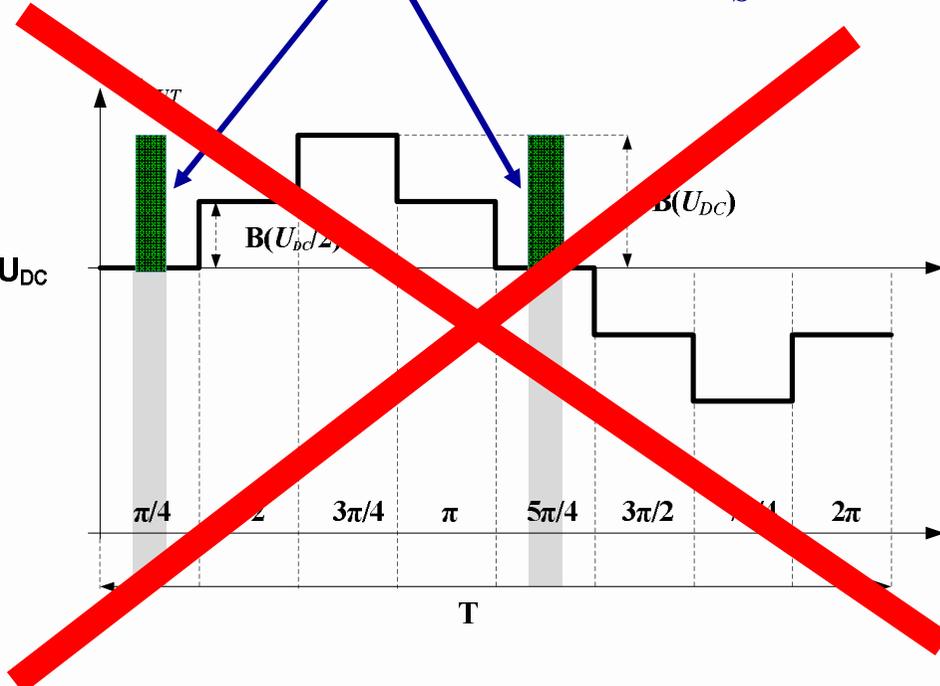


$$B = \frac{U_{DC}}{U_{IN}}$$


$$\frac{t_N}{T} + \frac{t_S}{T} = D_N + D_S = 1$$

# Modulation Technique

## 3L-NPC-qZSI

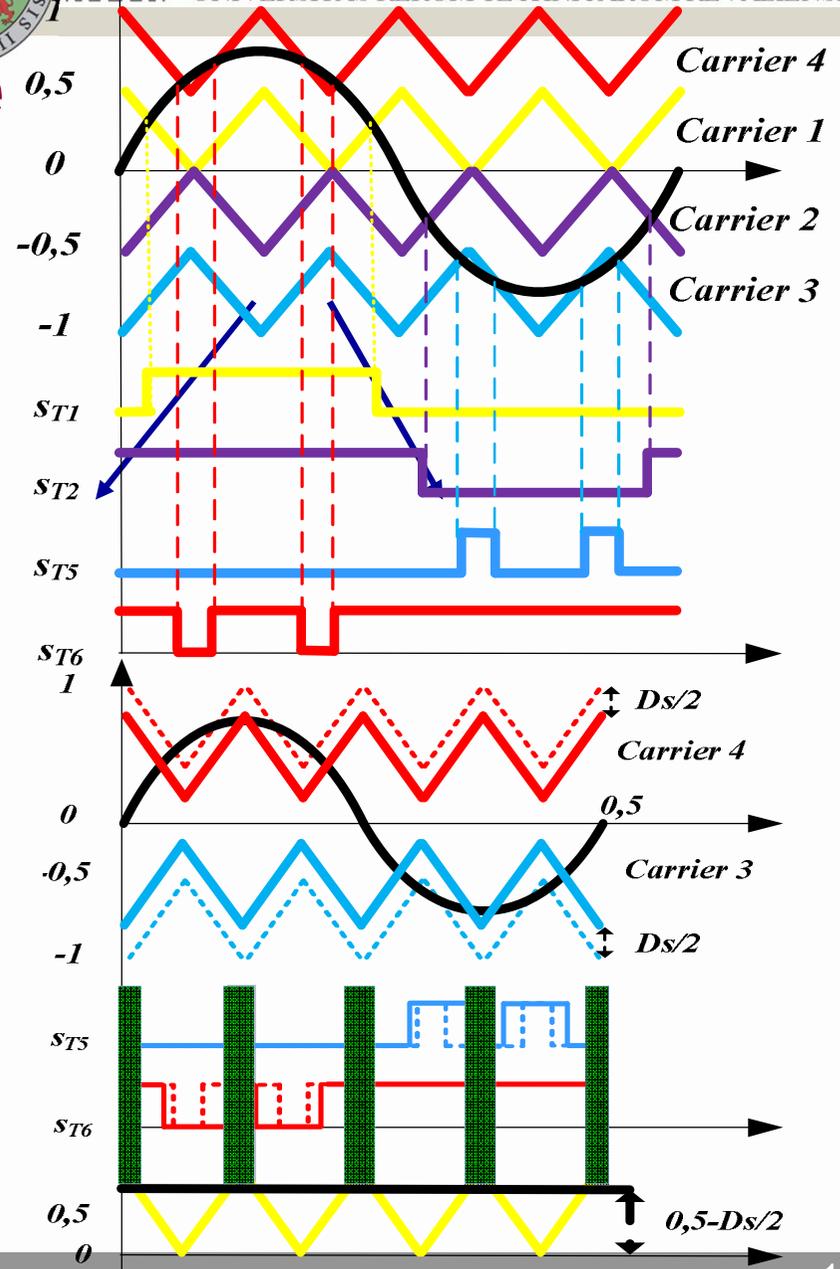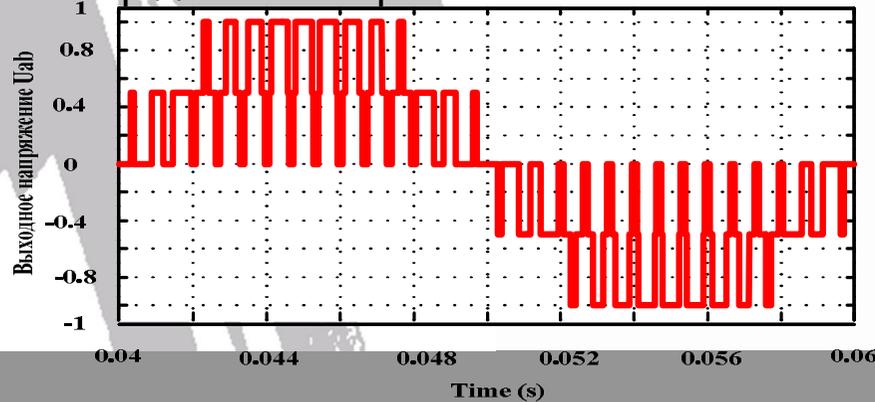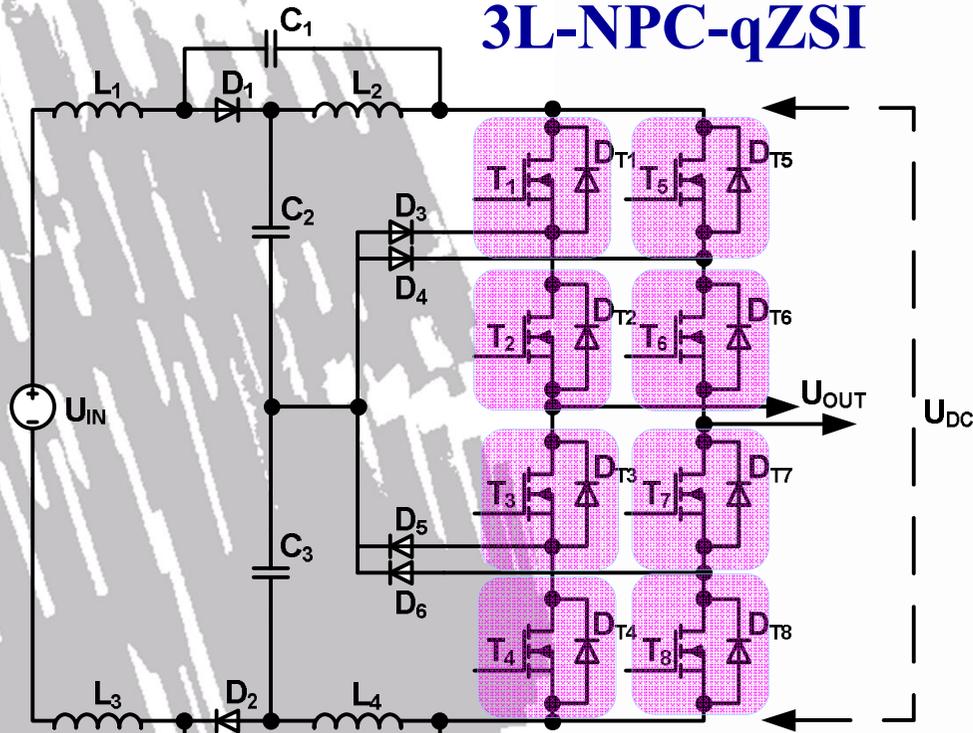


# Steady State Analyses. CCM conditions

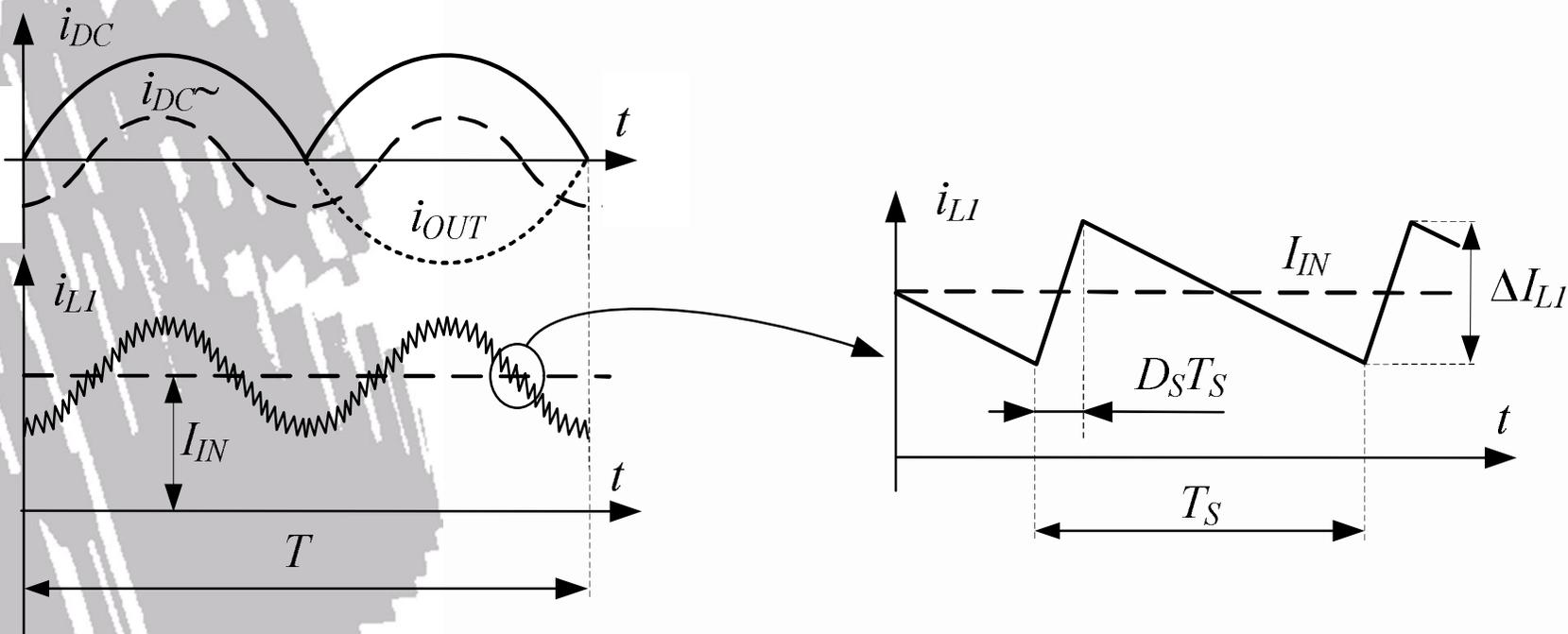


There are two components of current ripple: high switching frequency ripple and 100 Hz (single phase) ripple
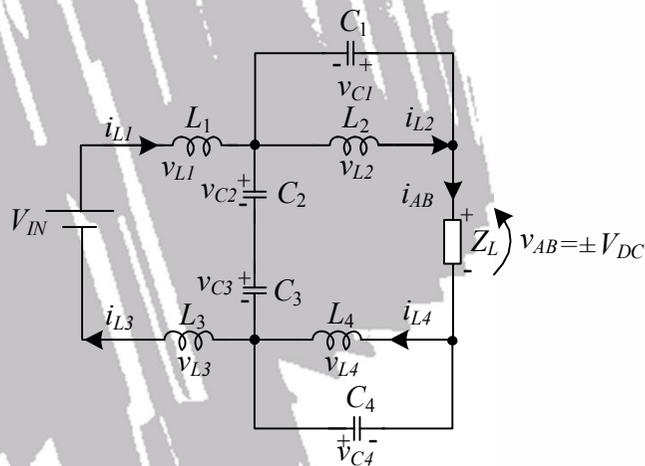
# Steady State Analyses. Equivalent circuits


Equivalent circuit for 100 Hz  
(single phase) ripple



Non shoot through

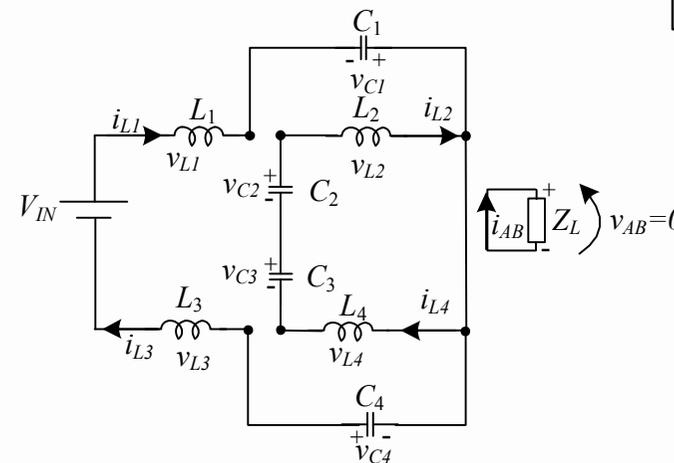

Shoot through

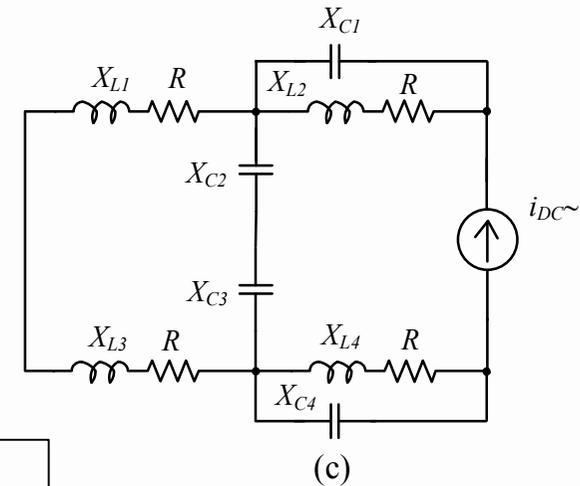

Equivalent circuits for switching ripple

# Steady State Analyses. Analytical equations

Boost Factor:  $V_{OUT\_MAX} = V_{IN} \cdot \frac{1 - D_S}{(1 - 2 \cdot D_S)}$

$$V_{C2} = V_{C3} = \frac{V_{IN} \cdot (D_S - 1)}{4 \cdot D_S - 2}$$

Capacitors:


$$K_{CL1} = \frac{v_{C1\sim}}{V_{C1}} = \frac{4}{3 \cdot \pi^2} \cdot \frac{P_{OUT} \cdot (1 - D_S) \cdot T^3}{V_{OUT}^2 \cdot D_S \cdot |16\pi^2 \cdot C_1^2 \cdot L_2 - T^2 \cdot C_1|}$$

$$V_{C1} = V_{C4} = \frac{D_S \cdot V_{IN}}{2 - 4 \cdot D_S}$$

Inductances:


$$K_{LL1} = \frac{i_{L1\sim}}{I_{IN}} = \frac{i_{L1\sim} \cdot V_{IN}}{P_{OUT}} = \frac{8}{3 \cdot \pi} \cdot \frac{(1 - 2 \cdot D_S) \cdot T^2}{(1 - D_S) \cdot (16\pi^2 \cdot C_2 \cdot L_1 - T^2)}$$
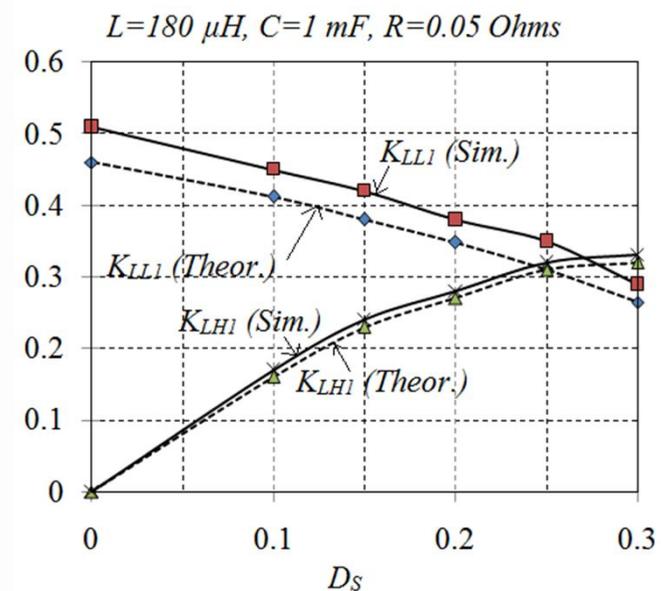
$$K_{LH1} = \frac{\Delta I_{L1}}{2 \cdot I_{IN}} = \frac{V_{OUT}^2 \cdot (1 - 2 \cdot D_S)}{2 \cdot (1 - D_S) \cdot L_1 \cdot P_{OUT}} T_S \cdot D_S$$




# Experimental Prototype

Control Unit (FPGA)	Cyclone IV EP4CE15E22C8
Input DC voltage $U_N$	220-440 V
Output power	2800 W
Nominal output AC voltage $U_{OUT}$	230 V
Capacitance value of the capacitors $C_1, C_4$	4000uF
Capacitance value of the capacitors $C_2, C_3$	1000 uF
Inductance value of the inductors $L_1... L_4$	145uH
Inductance of the inverter filter inductor $L_{f1}$	560uH
Inductance of the grid filter inductor $L_{f2}$	200 uH
Capacitance of the filter capacitor $C_f$	0,47uF
Switching frequency	100 kHz
PV panels	LDK 185D

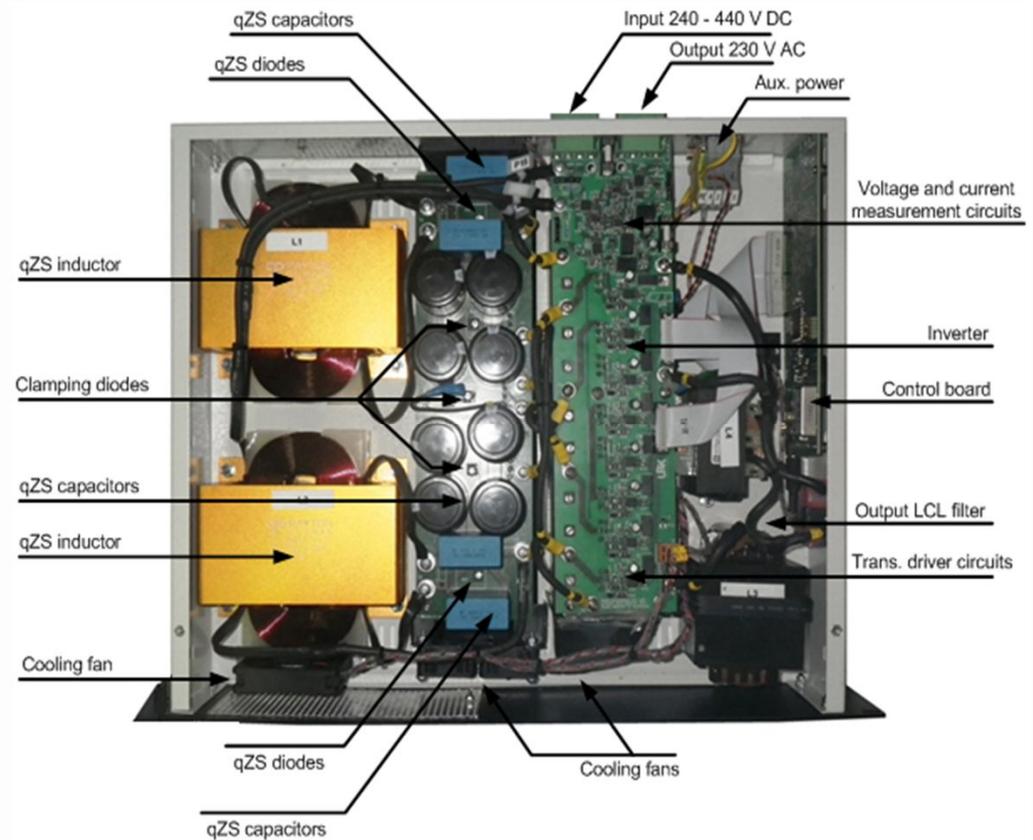

# Selected Components: transistors

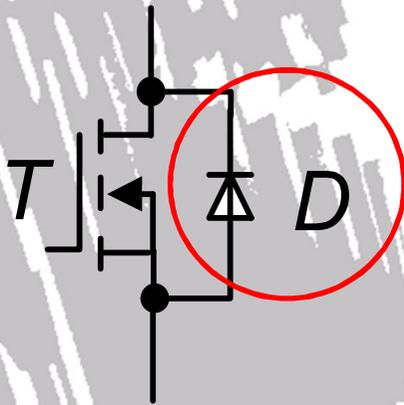

- **FCH47N60NF (FAIRCHILD)**
- $R_{DS(on)} = 57.5\text{m}\Omega$ ,  $I_D = 23.5\text{A}$
- 
- Total Gate Charge 121 nC
- $dv/dt = 50\text{ V/ns}$
- Reverse Recovery Time 169 ns
- Reverse Recovery Charge 1.3  $\mu\text{C}$
- **IPW65R080CFD (Infineon)**



1918


TALLINNA TEHNIKAÜLIKOOL

UNIVERSITAS RERUM TECHNICARUM REVALIENSIS



# Selected Components: qZS and clamped diodes

- **C3D20060D (Cree)**
- Repetitive Peak Reverse Voltage V600V
- Continuous Forward Current 28 A
- Total Capacitive Charge 20 nC



# Experimental results

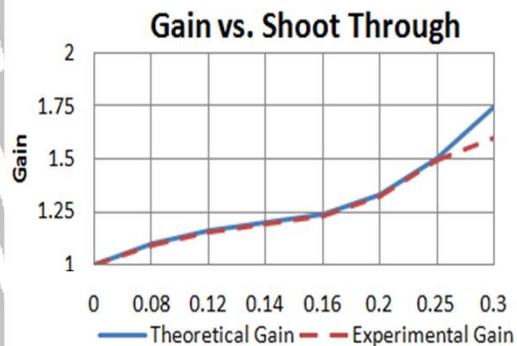

(a)

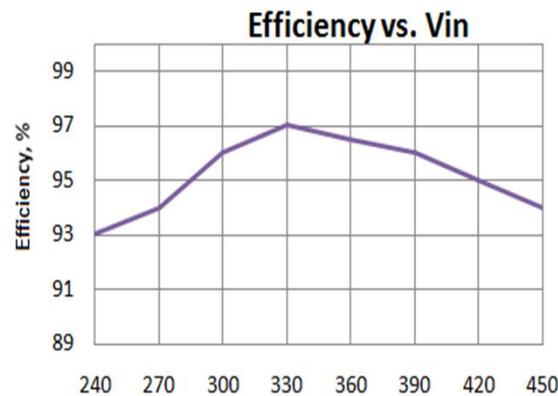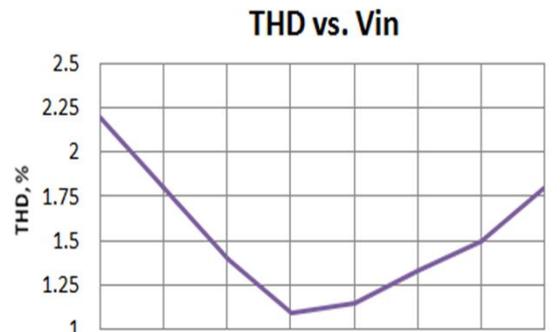


(b)

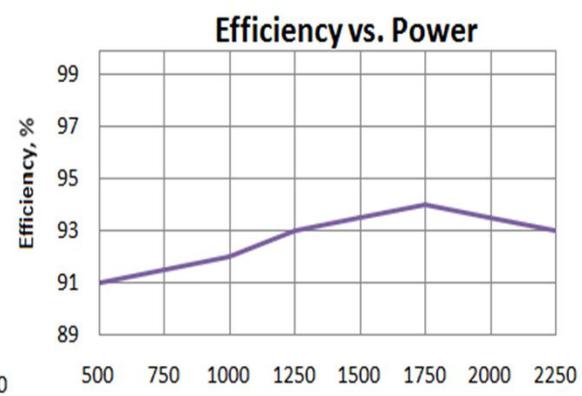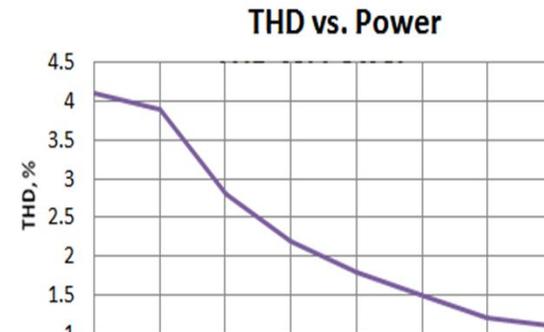


(c)
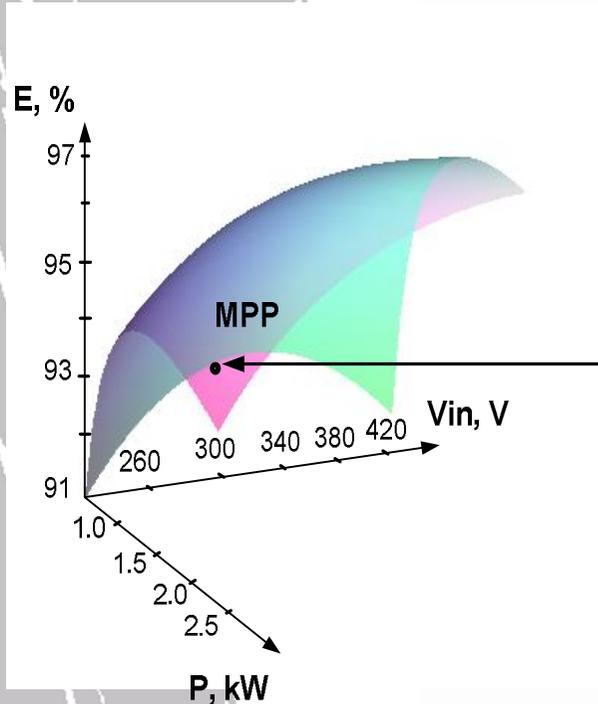
# Experimental results. Losses distribution.



(a)

## Losses Estimation


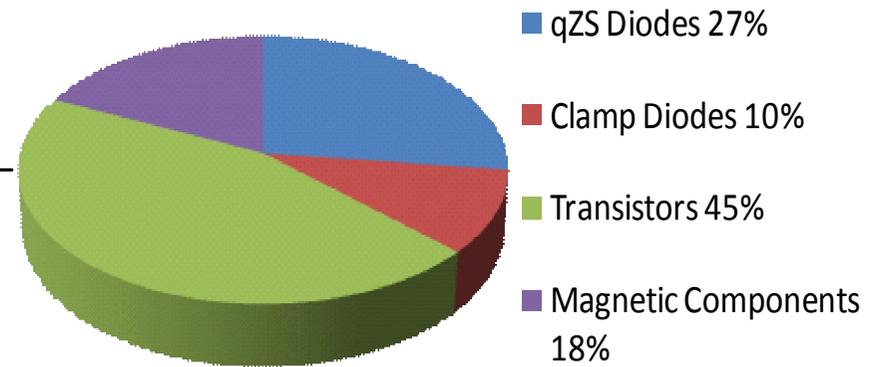


Maximum Power Point: 250 V,  
2100W, 94% efficiency


(b)

# Experimental Results in Spain with PV panels

Working Point	1	2	3	4
V <sub>pv</sub> , V	227	234	241	249
Power, W	1200	1500	1800	2100
THD, %	2.2	1.8	1.5	1.1
Efficiency, %	92	93	94	93

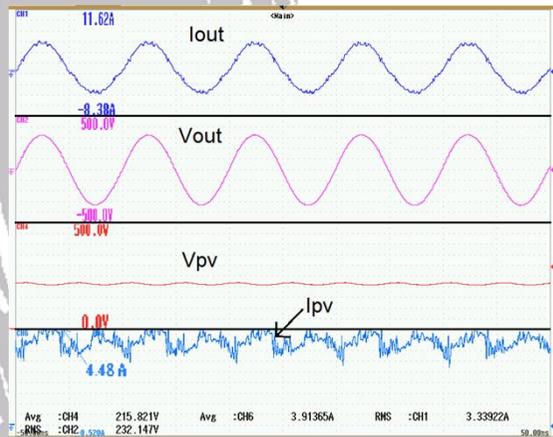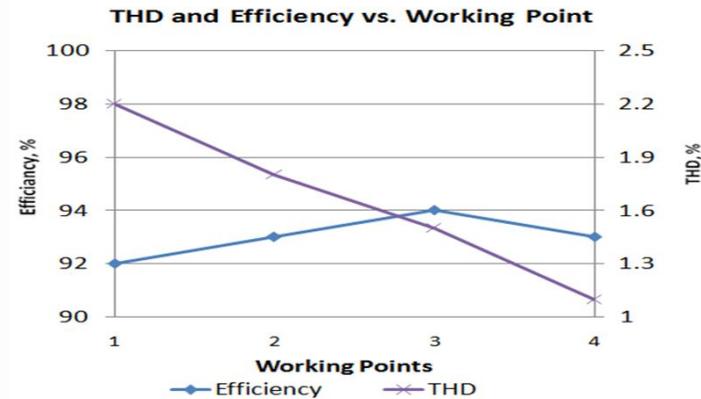

7 serial panels

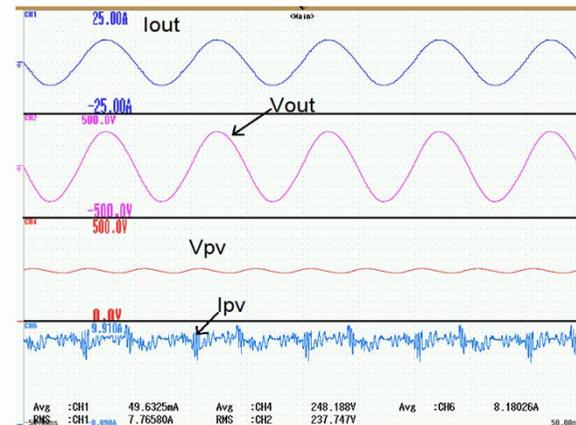

7x2 serial panels

# Conclusions:

- 3L-NPC qZS single phase inverter was proposed and designed (3kW).
- Features: wide input voltage range (220V - 450V), CCM of the input current (20% ripple).
- A sufficiently high converter efficiency (94-97%) was achieved through the use of modern electronic components, such as Schottky diodes based on silicon carbide and power switches with low gate charge and barrier capacitance reverse.

# Further Research Activity



3 kW 3-phase 3L NPC qZSI  
project financed by ECPE!

# Thank you for attention!

## Questions?

