

International Power Conversion and Drive Colloquium  
IPCDC-2013, Moscow, October 16, 2013

# Multilevel Boost Converters, their Applications, Comparisons and Practical Design Aspects

***Valery Meleshin***

*R&D Group Manager, JSC "Electro C"*

[V.Meleshin@sipower.ru](mailto:V.Meleshin@sipower.ru)

***Rais Miftakhutdinov***


*Technologist, Texas Instruments Inc.*

[r-miftakhutdinov1@ti.com](mailto:r-miftakhutdinov1@ti.com), [rais@ieee.org](mailto:rais@ieee.org)


# Outline

- 1. Power Systems with Boost DC-DC Converters**
- 2. Low Cost, High Efficiency and Density driving Technologies**
- 3. Three-level Boost Topologies:**
  - a) Flying Capacitor**
  - b) Diode Clamped**
- 4. Multi-level Topologies**
- 5. Experimental Results**
- 6. Conclusion and Acknowledgments**
 
# Power Generation and Distribution System with Intermediate DC Bus


 
# Power Conversion and Flow in HEV Powertrain




# *Key Vectors for Low Cost, High Efficiency and Density Solution*

- **Optimal Power System**
- **Topology**
- **Components and Materials**
  - **New SiC and GaN Power Devices**
  - **Isolated Driver Technique**
  - **New Passives: Capacitors and Magnetics**

# Key Parameters of Semiconductor Materials

Material	Si	GaAs	InP	GaN	4H-SiC
Bandgap, eV	1.1	1.43	1.35	3.4	3.26
Breakdown Field, V/ $\mu\text{m}$	30	40	50	300	200-<300
Electron Mobility, $\text{cm}^2/\text{Vs}$	1500	8500	5400	1500	700
Saturated Electron velocity, $10^7$ cm/s	1	<1.0	1	1.3	2
Peak Electron velocity, $10^7$ cm/s	1	2.1	2.3	2.5	2
Thermal Conductivity, W/cmK	1.3	0.55	0.68	>1.5	<3.8
Lattice Constant (a), $\text{\AA}$	5.43	5.65	5.87	3.19	3.07
Dielectric Constant, $\epsilon_r$	11.7	12.9	12.5	9	9.7

 
# Specific $R_{dson}$ vs $V_{break}$ of Si, GaN and SiC




# Key Parameters of Commercial SiC Transistors

Vendor	Part	Vds, V	Id, A	Vg, V	Rdson , mΩ	Qg, nc	FM, mΩ•nc	Die size, mm x mm	Spec. Ron. mΩ•mm <sup>2</sup>
Cree	CPM2-1200-0080B	1200	20	+25/-10	80	49	3920	3.36x 3.1	833
Cree	CPM2-1200-0025B	1200	50	25/-10	25	179	4475	6.44x4.0 4	650
Rohm	SCT2080KE	1200	35	+22/-6	80	106	8480	TO-247	n/a
GeneSic	GA50JT12-247 (bipolar)	1200	50	3.3V, 2A	28	n/a	n/a	TO-247	n/a
MicroSemi	APTMC120AM55CT1 AG	1200	55	+25/-10	49	98	4802	Module	n/a
ST Micro	SCT30N120	1200	45	+25/-10	80	105	8400	HiP247	n/a

 
# Signal and Bias Isolation Need for Multilevel Topologies


 
# Electrical Diagram of Signal and Bias Isolation Driver Board



# Isolated Driver Board View



 


**Driver IC  
UCC27532**

**Bias  
Supplies**

**Opto-  
Coupler**
   
# Three-level Flying Capacitor Boost Converter



**TFR for Non-overlapping control**

$$V_o = \frac{2V_{in}}{2-D}$$

**TFR for Overlapping control**


**Version a)**

$$V_o = \frac{2V_{in}}{1-D}$$

**Version b),  $0 \leq k \leq 1$**


$$V_o = \frac{2V_{in}}{(1-D)(2-k)}$$

# Three-level Boost Converter

 


$$V_o = 2V_c = 2V_{in} / (2 - D) \quad \text{TFR for control a)}$$
 
$$V_o = 2V_c = 2V_{in} / (1 - D) \quad \text{TFR for control b)}$$



**a) Non-overlapping control**

 


**b) Overlapping control**


# Comparison of TLFCBC vs TLBC

Circuit	Mode	Capacitor	$I_{rms} / I_{load}$
TLBC	Without overlapping	C1 (C2)	$\sqrt{D/(2-D)}$
	With overlapping		$\sqrt{(1+D)/(1-D)}$
TLFCBC	Without overlapping	C1	$2\sqrt{D}/(2-D)$
	With overlapping		$2/\sqrt{1-D}$
	Without overlapping	C2	$\sqrt{D/(2-D)}$
	With overlapping		$\sqrt{(1+D)/(1-D)}$


## Core loss: BC vs TLBC

 


## Capacitor RMS current: overlapping

 
 
## Capacitor RMS current: non-overlapping


 
# Four-level Flying Capacitor Boost Converter



**TFR for Non-overlapping control**

$$V_o = 3V_{in} / (3 - 2D)$$

**TFR for Overlapping control**

$$V_o = 3V_{in} / (1 - D)$$

**TFR for N-level converter with non-overlapping control**


$$V_o = NV_{in} / (N - (N - 1)D)$$

**TFR for N-level converter with overlapping control**

$$V_o = NV_{in} / (1 - D)$$

$D = t_i / (T / N)$       - Definition of D
 
# The same TFRs valid for Four-level Boost Converter



$$D = t_i / (T / N) \quad \text{- Definition of D}$$

**TFR for Non-overlapping control**

$$V_o = 3V_{in} / (3 - 2D)$$

**TFR for Overlapping control**

$$V_o = 3V_{in} / (1 - D)$$


**TFR for N-level converter with non-overlapping control**

$$V_o = NV_{in} / (N - (N - 1)D)$$


**TFR for N-level converter with overlapping control**

$$V_o = NV_{in} / (1 - D)$$

 
# Prototype: Input 50V to 150V, Output 400V, 3kW



Start up waveform

 

 Efficiency vs input voltage at different Pout



# *Conclusion and Acknowledgements*

This topic is an attempt to outline key directions, solutions and implementations in Power using **multilevel boost converter and its supporting technologies.**

Obviously this talk is based on work and collective efforts of **our colleagues at JSC “Electro C” and Texas Instruments** to whom we extend our special thanks!